

Question 1

Not answered

Points out of
5.00

Remove flag

Active-high decoders are maxterm generators.

Select one:

- ☐ True
- ☐ False

The correct answer is 'False'.


Question 2

Complete

 10.00 points out
of 10.00

Flag
question

Which memory component does the following circuit describe?



- ☐ a. D-Flip Flop
- ☒ b. J-K Flip Flop
- ☐ c. S-R Latch
- ☐ d. D-Latch
- ☐ e. T-Flip Flop

The correct answer is:
J-K Flip Flop


Question 3

Complete

 0.00 points out of 10.00

Flag question

Which Boolean expression describes the behavior of the following circuit?



- ☐ a. $F = X'.Y'.Z' + X.Y.Z'$
- ☐ b. $F = 1$
- ☐ c. $F = X'.Y'.Z + X.Y.Z$
- ☐ d. $F = 0$
- ☒ e. $F = X'.Y.Z' + X.Y.Z$

The correct answer is:

$$F = X'.Y'.Z + X.Y.Z$$

Question 4

Not answered

Points out of 10.00

Remove flag

For an S-R latch that is built by identical NOR gates, what is the expected behavior of the latch if we take the following actions: we set both input pins simultaneously, wait for a while and reset them simultaneously?

- ☐ a. The latch continuously outputs 0.
- ☐ b. The latch continuously outputs 1.
- ☐ c. None of these.
- ☐ d. The latch first outputs 1 then 0 and the output value remains 0.
- ☐ e. The latch first outputs 0 then 1 and the output value remains as 1.


The correct answer is:

None of these.

Question **5**

Not answered

Points out of
5.00

 Remove flag

The outputs of Mealy-type sequential circuits (Mealy Finite State Machines) are solely dependent on the state (memory) information of the circuits.

Select one:


- ☐ True
- ☐ False

The correct answer is 'False'.

Question **6**

Complete

5.00 points out
of 5.00

 Remove flag

All sequential circuits cannot be built by using only NOT and OR gates.

Select one:

- ☐ True
- ☒ False

The correct answer is 'False'.


Question 7

Not answered


Points out of
10.00

Remove flag

 Which one of the following statements is wrong for the circuits below?



(a) Circuit 1

 

(b) Circuit 2

- ☐ a. After setting $I1=0$, $I2=1$, both circuits output the value 0 ($Q=0$).
- ☐ b. After setting $I1=0$, and $I2=0$ on both circuits, the output values do not change.
- ☐ c. Both circuits could be used to build a D-flip flop by using additional AND and NOT gates.
- ☐ d. It is unsafe to set $I1=1$, $I2=1$ on both circuits.
- ☐ e. After setting $I1=1$, $I2=0$, both circuits output the value 1 ($Q=1$).

The correct answers are:

After setting $I1=1$, $I2=0$, both circuits output the value 1 ($Q=1$).


After setting $I1=0$, $I2=1$, both circuits output the value 0 ($Q=0$).

It is unsafe to set $I1=1$, $I2=1$ on both circuits.

Question 8

Not answered

Points out of
5.00

 Remove flag

D-type flip-flops are more suitable for automated design.

Select one:

- ☐ True
- ☐ False

The correct answer is 'True'.

Question 9

Not answered

Points out of
5.00

 Remove flag

Propagation delay of logic gates does not affect the maximum frequency value of a clock signal that is applied to a sequential circuit.

Select one:

- ☐ True
- ☐ False

The correct answer is 'False'.

Question 10

Complete

25.00 points out of 25.00

Flag question

Below characteristic tables of several memory components are given. Please match the tables with one of the memory components: D-Latch, D-Flip Flop, S-R Latch, J-K Flip Flop, and T-Flip Flop.

Inputs		Output
IO		$Q(t)$
0		$Q(t-1)$
1		$Q'(t-1)$

T-Flip Flop ⇅

Inputs		Output
IO		$Q(t)$
0		0
1		1

D-Flip Flop ⇅

Inputs		Output
II	IO	$Q(t)$
0	0	$Q(t-1)$
0	1	0
1	0	1
1	1	-

S-R Latch ⇅

Inputs		Output
II	IO	$Q(t)$
0	0	$Q(t-1)$
0	1	0
1	0	1
1	1	$Q'(t-1)$

J-K Flip Flop ⇅

Inputs		Output
II	IO	$Q(t)$
0	0	$Q(t-1)$
0	1	0
1	0	$Q(t-1)$
1	1	1

D-Latch ⇅

The correct answer is:

Inputs		Output
10		$Q(t)$
0		$Q(t-1)$
1		$Q'(t-1)$

→ T-Flip Flop,

Inputs		Output
10		$Q(t)$
0		0
1		1

→ D-Flip Flop,

Inputs		Output
11	10	$Q(t)$
0	0	$Q(t-1)$
0	1	0
1	0	1
1	1	-

→ S-R Latch,

Inputs		Output
11	10	$Q(t)$
0	0	$Q(t-1)$
0	1	0
1	0	1
1	1	$Q'(t-1)$

→ J-K Flip Flop,

Inputs		Output
11	10	$Q(t)$
0	0	$Q(t-1)$
0	1	0
1	0	$Q(t-1)$
1	1	1

→ D-Latch

Question **11**

Complete

5.00 points out of 5.00

🚩 Flag question

One important advantage of using JK-type flip-flops when sequential circuits are designed manually is that the combinational circuitry that determines the values of their inputs is likely to be simpler.

Select one:

- ☒ True
- ☐ False

The correct answer is 'True'.

Question **12**

Complete

5.00 points out of 5.00

🚩 Flag question

Designing sequential circuits with D-type flip flops is complicated by the fact that the input equations for the flip flops must be derived indirectly from the state table.

Select one:

- ☐ True
- ☒ False

The correct answer is 'False'.